

17353

21314

3 Hours / 100 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answers with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

SECTION - I

- 1. Solve any NINE of the following:** **18**
- Draw the single line diagram of electrical power A.C. supply system from generation to distribution level.
 - Define regulation of transformer. Also write its formula.
 - State any two applications of transformers.
 - Compare A.C & D.C measuring instruments in any two aspects.

P.T.O.

- e) Draw circuit symbol of the following electrical components:
 - i) switch
 - ii) socket
 - iii) fan
 - iv) lamp.
- f) Write the meaning of energy audit.
- g) Write the working principle of 3 phase squirrel cage induction motor briefly.
- h) What is meant by electric heating ? Write any one application of it.
- i) Write the classification of lamps with their resting.
- j) Write the relationship of line and phase values of voltages and currents of star connected and delta connected systems.
- k) Draw the connection diagram of $I\phi$ energy motor.
- l) State any two applications of capacitor start and run 1 phase induction motor.
- m) Give the names of electrical machines used in agro system. (Any two).
- n) Draw the connection diagram of:
 - i) step up
 - ii) step down auto transformer.

2. Solve any **FOUR** of the following:

16

- a) Define following electrical terms:
 - i) frequency
 - ii) time period
 - iii) maximum value
 - iv) average value.
- b) Give constructional details and working principle of digital multimeter with neat sketch.

- c) Derive emf equation of 1 phase transformer.
- d) i) State the types of tariff.
ii) Write the names of different methods of power factor improvement.
- e) Why is the single phase induction motor not self starting motor ? Explain.
- f) Classify electrical drives based on their speed torque characteristics.

3. Solve any FOUR of the following:

16

- a) A circuit consists of resistance $R = 20 \Omega$ inductance of $L = 0.05H$. A source voltage of 230 volt, 50 Hz frequency is connected across the series combination of R and L.
Calculate following:
 - i) total circuit current
 - ii) total circuit impedance
 - iii) voltage across resistor
 - iv) voltage across inductor.
- b) With a neat sketch explain the working of a MI voltmeter.
- c) Explain the working principle of a 1 ϕ transformer with a neat sketch.
- d) Discuss how MCB & ELCB are used for the protection of electrical systems against the faults of the system.
- e) Describe the working of direct on line starter with neat sketch used for a 3 ϕ induction motor.
- f) State any four factors for the selection of motors for different electrical drives.

SECTION - II

- 4. Attempt any SEVEN of the following:** **14**
- a) List any two application of capacitor.
 - b) Sketch the symbol of SCR. Name different terminals.
 - c) Draw transistor output characteristics in common emitter configuration.
 - d) State the need of voltage regulator circuit.
 - e) Define negative logic with respect to digital circuit.
 - f) Sketch V-I characteristics of Si and Ge PN junction diode on same scale.
 - g) List any two application of TRIAC.
 - h) Draw symbol of NPN and PNP transistor.
 - i) Give formula of D.C. output voltage for:
 - i) Half wave rectifier.
 - ii) Full wave rectifier.
 - j) List two types of LED display.
- 5. Attempt any FOUR of the following:** **12**
- a) Draw and explain energy band diagram of insulator.
 - b) Explain construction of TRIAC.
 - c) Draw circuit diagram of single stage CE amplifier. State the role of coupling capacitor and bypass capacitor.
 - d) Explain working principle of zener shunt regulator.
 - e) Explain working of fullwave bridge type rectifier.
 - f) State and prove Demorgan's first theorem.

6. Attempt any FOUR of the following:**12**

- a) With neat sketch explain working principle of LED.
- b) Explain V-I characteristics of SCR in forward direction.
- c) Explain need of power amplifiers. State its types.
- d) Compare half wave rectifier and full wave rectifier (center tapped) with respect to following point:
 - i) No. of diode used
 - ii) PIV of diode
 - iii) Ripple factor.
- e) Using boolean algebra prove that:
$$(A + B) (A + C) = A + BC$$
- f) Implement OR gate using only NAND gate.

7. Attempt any FOUR of the following:**12**

- a) Explain formation of N-type semiconductor.
 - b) Explain working of zener diode in reverse bias condition.
 - c) Explain operation of an NPN bipolar junction transistor.
 - d) Draw and explain block diagram of power supply.
 - e) Sketch the diagram of LC and π (pi) filter. Which circuit is better ? Why ?
 - f) Draw symbol, truth table and write logic expression for:
 - i) EX-OR gate
 - ii) NOR gate.
-

17353

21314

3 Hours / 100 Marks
