

**17321****21314**

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--

- Instructions :** (1) **All** questions are **compulsory**.
(2) Answer each next main question on a **new** page.
(3) Illustrate your answers with neat sketches **wherever** necessary.
(4) Figures to the **right** indicate **full** marks.
(5) Assume suitable data, if **necessary**.
(6) Mobile Phone, Pager and any other Electronic Communication devices are **not permissible** in Examination Hall.

MARKS1. A) Attempt **any six** of the following :**12**

- Define knee voltage and reverse saturation current of diode.
- List various transistor biasing methods.
- Define α and β of transistor.
- Draw a functional pin diagram of IC 723.
- Draw logic symbol and truth table of OR gate and EX-NOR gate.
- State Barkhausen criteria for oscillation.
- Draw the symbol and list one application of :
 - Schottkey diode
 - Varactor diode.
- Give four applications of digital electronics.
 - What is filter ? List the types of filter.

B) Attempt **any two** of the following :**8**

- Draw experimental set up to obtain forward characteristics of p-n junction diode. Draw forward characteristics and explain it.
- Compare full wave rectifier and half wave rectifier (4 points).
- Describe the operation of npn transistor with diagram.

P.T.O.

**MARKS**

2. Attempt **any four** of the following : **16**
- a) Draw forward and reverse characteristics of zener diode with neat circuit diagram.
 - b) Draw the circuit diagram of Bridge Rectifier with π filter. Draw its input and output waveforms.
 - c) Describe transistor as a switch with neat sketch.
 - d) Derive the relationship between α and β .
 - e) Describe the operation of p-channel FET with diagram.
 - f) Describe the operation of zener diode as voltage regulator with diagram.
3. Attempt **any four** of the following : **16**
- a) Describe the working principle of LED with diagram.
 - b) A CE configuration of transistor if $\beta = 100$, leakage current $I_{CEO} = 150 \mu A$, $I_B = 0.2 mA$. Calculate I_C and I_E .
 - c) Draw V_E - I_E characteristics of UJT. Describe the different regions on characteristics.
 - d) Compare BJT and FET (4-points).
 - e) Describe the operation of transistorized shunt regulator with diagram.
 - f) Draw the block diagram of microprocessor. State the function of each block.
4. Attempt **any four** of the following : **16**
- a) Differentiate between Class A and Class B power amplifier (4-points).
 - b) Describe the working principle of LASER diode with diagram.
 - c) Draw input and output characteristics of CE configuration and shows various regions on characteristics.



MARKS

- d) Draw the circuit diagram of single stage CE amplifier. Give the function of each components.
- e) Define the terms related to FET :
 - i) Drain resistance
 - ii) Transconductance
 - iii) Amplification factor
 - iv) Pinchoff voltage.
- f) Draw the circuit diagram of dual regulator using regulator IC's 7812 and 7912 and give the function of each components.

5. Attempt **any four** of the following :

16

- a) Describe the operation of N-channel enhancement type MOSFET with diagram.
- b) Draw the circuit diagram of two stage transformer coupled amplifier. Give advantages and disadvantages of it.
- c) Describe voltage divider bias method with the help of diagram.
- d) An AC supply of 230 V is applied to half wave rectifier circuit. A transformer turns ratio is 10 : 1. Find :
 - i) Output DC voltage
 - ii) Peak inverse voltage.
- e) Draw the circuit diagram of Hartley oscillator and give the function of each components.
- f) Describe how the oscillations are maintained in crystal oscillator with diagram.

**MARKS**

6. Attempt **any four** of the following :

16

- a) Draw the circuit diagram of RC phase shift oscillator. Derive the equation for frequency oscillation.
 - b) Draw the circuit diagram of colpitts oscillator. A colpitt oscillator has $C_1 = 250 \text{ PF}$, $C_2 = 100 \text{ PF}$ and $L = 60 \mu \text{ H}$. Find the value of frequency of oscillation.
 - c) Why NOR gate is called universal gate ? Implement OR, AND gate using NOR gate.
 - d) Draw the block diagram of DC power supply. Give the function of each block.
 - e) Describe the operation of two stage R-C coupled amplifier with diagram.
 - f) Comparison between CB and CC configuration of transistor (4-points).
-