

**17321****14115**

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--

Instructions : (1) **All** questions are **compulsory**.(2) Illustrate your answers with **neat** sketches **wherever** necessary.(3) Figures to the **right** indicate **full** marks.(4) **Assume** suitable data, **if** necessary.(5) Mobile Phone, Pager and any other Electronic Communication devices are **not permissible** in Examination Hall.

MARKS1. Answer **any 10** of the following :**20**

- a) Define doping. State any 2 trivalent impurities.
- b) Draw V-I characteristics of PN junction diode and give the rated value of cut in voltage for Si and Ge.
- c) Compare LED and photodiode on basis of
 - a) Working principle
 - b) Biasing used
 - c) Symbol
 - d) Application.
- d) State the need of filters in a DC regulated power supply.
- e) Draw circuit diagram of transistor as a switch. State its voltage and current level in ON and OFF condition.
- f) Draw symbol of E-MOSFET (nch.) and D-MOSFET (n channel).
- g) State advantages of transistorized voltage regulator over Zener voltage regulator.
- h) Define bandwidth of an amplifier.
- i) State Barkhausen's criteria for sustained oscillations.
- j) Convert :
 - i) $(256)_D = ()_B$
 - ii) $(6A)_H = ()_D$

P.T.O.

**MARKS**

- k) Draw symbol of AND gate. State its truth table and write its Boolean expression.
- l) State the meaning of cross-over distortion w.r. to class B push pull amplifiers.
- m) Draw characteristics of UJT and label its regions.
- n) Which BJT biasing circuit is popularly used ? State the reason why it is used.

2. Attempt any four of the following :**16**

- a) Differentiate between BJT and FET on basis of
 - i) Input impedance
 - ii) Control factor
 - iii) Bipolar/Unipolar
 - iv) Thermal stability.
- b) Draw and state the working principle of LED with neat well labeled diagram.
- c) Draw symbol of point contact diode. State its working principle. Give any two applications.
- d) Draw circuit diagram of full wave centre tap rectifier with LC filter along with its input/output waveforms.
- e) Draw circuit diagram of Hartley oscillator. Give function of each component in it. State its frequency equation.
- f) State advantages and disadvantages of transistorised series voltage regulator (any four points).

3. Attempt any four of the following :**16**

- a) Differentiate between class A and class B amplifier on basis of :
 - a) Q-point
 - b) Collector current waveform
 - c) Distortion
 - d) Efficiency.
- b) Sketch typical UJT characteristics. Label each region and all important points on the characteristics.
- c) Construct OR gate using NAND gate.



MARKS

- d) Draw and explain frequency response of single stage amplifier.
- e) Draw symbol of varactor diode. State reason why it is called vari-cap.
- f) What is the need of a regulated power supply ? Define load and line regulation with ref. to regulator.

4. Attempt **any four** of the following : **16**

- a) State the principle of crystal oscillator. Draw circuit diagram of a crystal oscillator. Give its working with respect to the function of each component.
- b) Draw CE output characteristics. Label the regions in it and give application of each region.
- c) Draw circuit diagram of voltage divider biasing of BJT. How stability is achieved in Q-point.
- d) Draw transformer coupled class A power amplifier.
- e) State the three parameters of JFET. Give relation between them.
- f) Draw Zener diode as a voltage regulator. State the conditions in which voltage is stabilized.

5. Attempt **any four** of the following : **16**

- a) Draw basic block diagram of microprocessor. State function of each block in it.
- b) State application of digital systems. Draw a analog and digital signal. State its important features.
- c) With a neat circuit diagram, explain the principle of operation of RC phase shift oscillator.
- d) Draw pin diagram of 723. Give advantages of IC voltage regulators over discrete voltage regulators.
- e) Compare E-MOSFET and D-MOSFET on basis of : application, mode of operation, channel, symbol.
- f) Compare CB, CE, CC configuration on basis of voltage gain, current gain, input impedance, output impedance.



6. Attempt **any four** of the following :

16

- a) Draw and explain working principle of NPN transistor.
 - b) Compare HW, FW bridge and FW center tap on basis of PRV, ripple factor, efficiency, TUF.
 - c) State specifications of Zener diode. Draw symbol and characteristics of Zener diode. Label all regions in it.
 - d) Draw circuit diagram of 2 stage direct coupled amplifier. Explain its frequency response.
 - e) List types of amplifier coupling. Draw circuit diagram of amplifier used in Audio frequency range. Explain the components used in it.
 - f) Draw circuit diagram of a bridge rectifier. State function of diode and working in both the half cycles with waveforms.
-