



MAHARASHTRA STATE BOARD OF TECHNICAL EDUCATION
(Autonomous)
(ISO/IEC – 27001 – 2005 Certified)


WINTER – 12 EXAMINATION


Model Answer

Subject Code : **12058**

Page No. : 1 / 21


Q1 .	Attempt any Ten	20 Marks
Ans.a	<p>PIV – Peak Inverse Voltage</p> <p>It is the maximum reverse voltage that a diode can withstand in the reverse direction without breaking down.</p> <p>TUF – Transformer Utilization Factor</p> <p>It is defined as the ratio of DC Power delivered to the load to the ac rating of the transformer secondary.</p> <p>$TUF = \frac{\text{DC power delivered to the load}}{\text{AC rating of transformer secondary}}$</p>	<p>1</p> <p>1</p>
Ans.b	<p>i) Very good load regulation</p> <p>ii) Ripple factor is low</p> <p>iii) Filter is suitable for light as well as heavy load.</p> <p>iv) Diodes do not carry surge currents.</p> <p>v) Ripple factor does not depend on type of load.</p> <p>vi) LC filter provides continuous load current.</p>	Any 4, each carrying ½ mark.
Ans.c	<p>α - It is defined as the ratio of collector current I_C to the emitter current I_E</p> <p>$\alpha_{dc} = \frac{I_C}{I_E}$ or $\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$</p> <p>$\beta$ – It is defined as the ratio of collector current I_C to the Base Current I_B</p> <p>$\beta_{dc} = \frac{I_C}{I_B}$ or $\beta_{ac} = \frac{\Delta I_C}{\Delta I_B}$</p>	<p>1</p> <p>1</p>
Ans. d	<p>Regulator – The Voltage Regulator is a circuit that will give a constant output voltage inspite of changes in its input voltage or load current (I_L). Need of Regulator</p> <p>i) To maintain constant output voltage inspite of input voltage variation</p> <p>ii) To maintain constant output voltage inspite of I_L changes.</p>	<p>1</p> <p>1</p>
Ans. e	Typical Gain of Single Stage Amplifier is around 100-200. If gain more than 100-200 is required, then a multistage amplifier is used to provide higher gain.	2

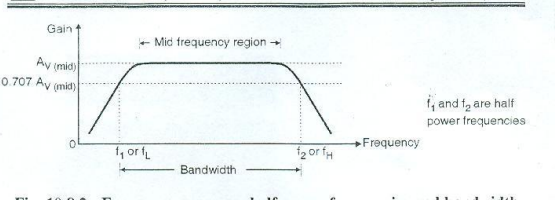Ans j	<p>4 specifications of Photo Transistor –</p> <ul style="list-style-type: none"> i) Collector Current ii) Collector dark current iii) Peak Wavelength iv) Rise time v) Collector – Emitter Breakdown Voltage vi) Power dissipation vii) Responsivity viii) Spectral Response ix) Quantum Efficiency x) Gain 	Any 4 points ½ mark each.
Ans k	<p>Bandwidth – It is defined as the difference between the half-power frequencies.</p> $BW = f_2 - f_1 \text{ Hz}$ <p>$f_1 \rightarrow$ lower cut off frequency</p> <p>$f_2 \rightarrow$ upper cut off frequency</p> <p>OR</p> <p>It is defined as the frequency Range over which the voltage gain of the amplifier remains almost constant.</p> 	2
Ans: l	<p>Names of Regulator IC's</p> <ul style="list-style-type: none"> 1) 78XX – fixed Positive Voltage Regulators. Eg. 7805, 7806, 7808, 7812, 7815, 7818, 7824. 2) 79XX – fixed Negative Voltage Regulators Eg. 7905, 7906, 7908, 7912, 7915, 7918, 7924. 3) IC 723 – General Purpose Regulator. 	2 marks – any 2 regulator IC

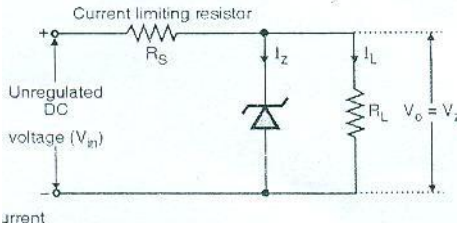Q2.	Attempt any 4	16 marks
Ans a	<p data-bbox="395 152 837 190">Zener Diode as Voltage Regulator</p>  <ul style="list-style-type: none"> - A Voltage Regulator circuit provides constant O/P voltage inspite of changes in its i/p voltage or load current. - The Series Resistance R_S is connected to limit the total current drawn from the unregulated power supply. - Zener diode is a shunt type voltage regulator because the zener diode is connected in parallel with the load resistance and is connected in reverse biased condition. - If V_{in} is higher than V_Z and if the I_Z is between I_{Zmin} & I_{Zmax} then the voltage across zener will remain constant equal to V_Z irrespective of any changes in V_{in} & I_L. As output voltage is constant and equal to V_Z, a regulated o/p voltage is obtained. - When V_{in} varies Assume R_L constant, V_{in} is varying So, I_L is also constant as $I_L = V_Z/R_L$ But V_{in} changes & supply current also changes $I = \frac{V_{in} - V_Z}{R_S}$ Also $I = I_Z + I_L$ If V_{in} is increased, then current I will increase. But as V_Z is constant & R_L is also constant, the I_L will remain constant. - The increase in current I will increase I_Z but I_Z is less than I_{Zmax}. - Thus the output voltage will remain constant. - When I_L varies Assume V_{in} constant, R_L is variable. If R_L increases, I_L will decrease. But I is constant. $I = \frac{V_{in} - V_Z}{R_S}$ Also $I = I_Z + I_L$ Therefore with decrease in I_L, I_Z will increase. This can be continued without damaging the Zener diode as long as I_Z is less than I_{Zmax}, the O/P voltage will remain constant. 	<p data-bbox="1358 190 1497 369">1 mark for dia. + 3 marks for explanation.</p>


Ans. b

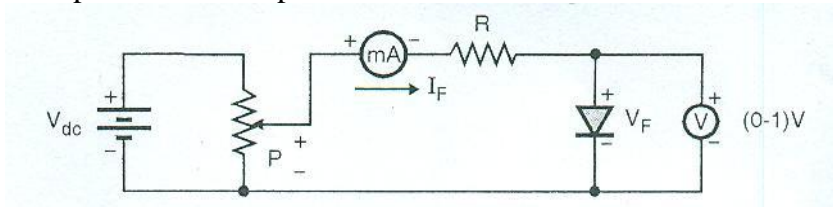Experimental set up for Forward Bias condition of diode



2


V-I Characteristics of diode

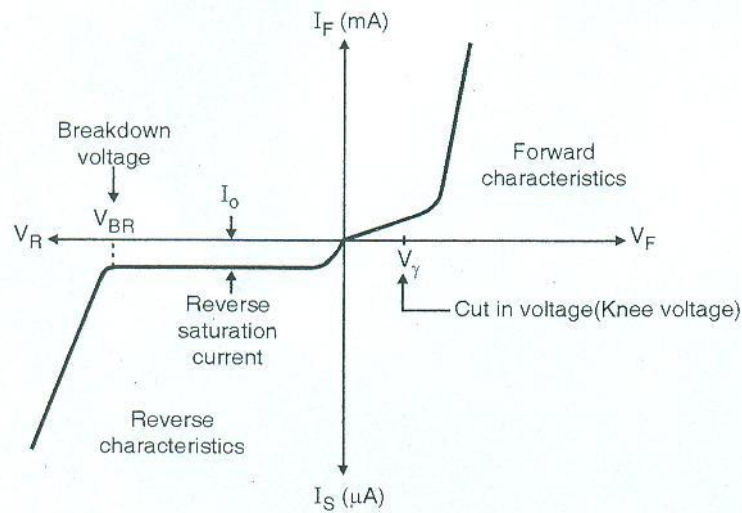

2


Ans : c

Input characteristics

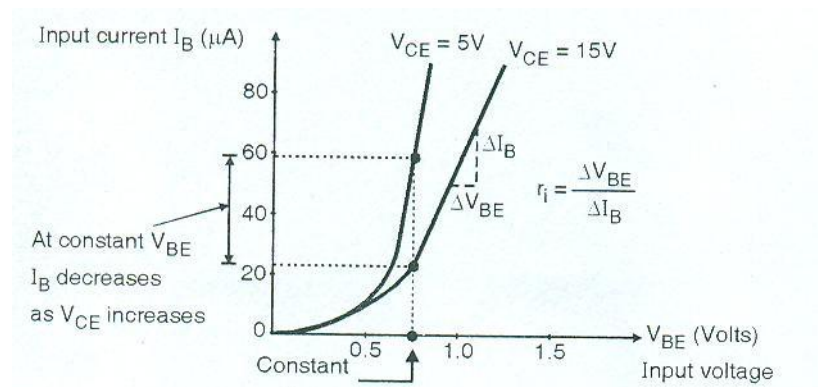



2

Output characteristics

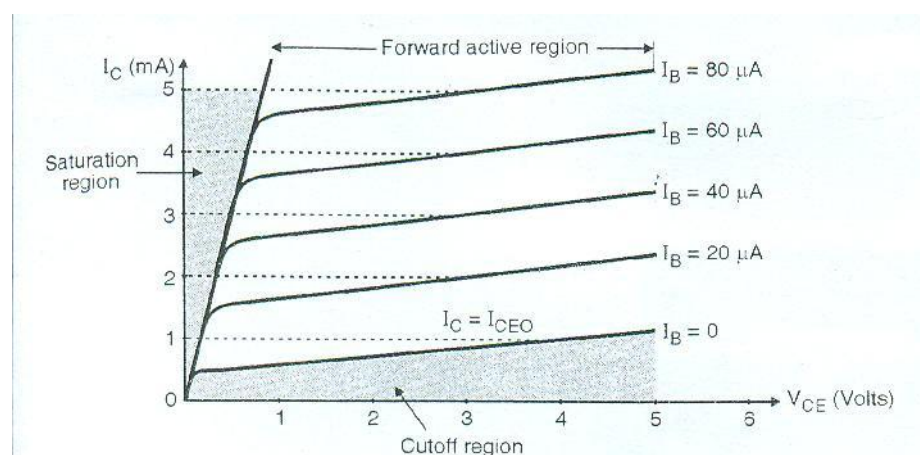


2

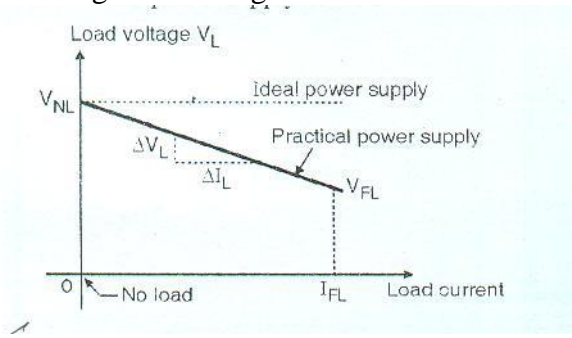Ans : e	<p>Load Regulation - It is defined as the change in output voltage when the load current is changed from zero (no load) to maximum (full load) value.</p> <p>It is calculated as</p> $\% \text{ Load Regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 \quad \left \begin{array}{l} V_{in} \text{ Constant} \end{array} \right.$ <p>Where V_{NL} = No load voltage ($I_L = 0$)</p> <p>V_{FL} = Full load voltage ($I_L = I_L \text{ Max}$)</p> <p>The percentage of Load Regulation of a power supply should ideally be equal to zero & practically it should be as small as possible.</p> <p>Load Regulation Diagram</p>  <p>Line Regulation : It is defined as the change in regulated load voltage for a specified range of line voltage with load R_L constant (I_L constant)</p> $\text{Line Regulation} = V_{HL} - V_{LL}$ <p>V_{HL} = Load voltage with high line voltage</p> <p>V_{LL} = Load voltage with low line voltage</p> <ul style="list-style-type: none"> - Ideally the line Regulation should be zero & practically it should be as small as possible. 	2
		2

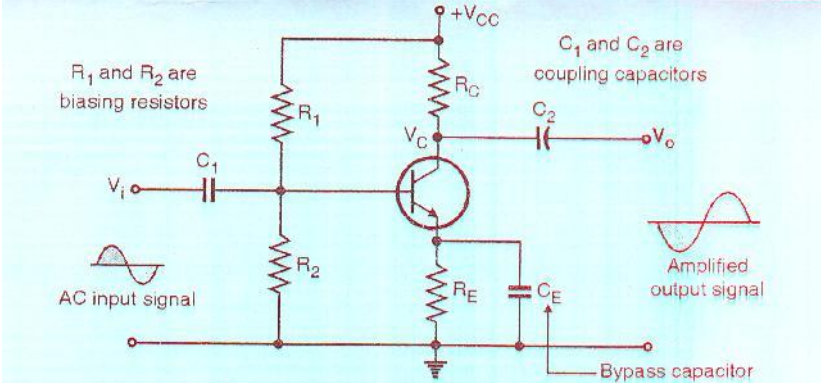Ans : f	<p>SINGLE STAGE TRANSISTOR AMPLIFIER</p>  <p>i) Biasing Circuit : The resistances R_1, R_2 & R_E, R_C, + V_{CC} & transistor form the dc biasing & stabilization ckts. The biasing ckt must establish a proper Q point otherwise a part of the –ve half cycle of the signal may be cut off in the o/p.</p> <p>ii) Input Capacitor (C_{in}) : An electrolytic capacitor $C_{in} = 10\mu\text{f}$ is used to couple the signal to the base of transistor. If it is not used, then signal source resistance will come across R_2 & thus change the bias. The capacitor C_{in} allows only a.c. signal to flow but isolates the signal source from R_2.</p> <p>iii) Emitter Bypass Capacitor C_E : An emitter bypass capacitor $C_E \cong 100\mu\text{F}$ is used in parallel with R_E to provide a low reactance path to the amplified ac signal. If it is not used then amplified ac signal flowing through R_E will cause a voltage drop across it, thereby reducing the o/p vg.</p> <p>iv) Coupling Capacitor C_C : The C_C coupling capacitor $\cong 10\mu\text{f}$ couples one stage amplification to next stage. If it is not used, the bias conditions of the next stage will be drastically changed due to the shunting effect of R_C. This is because R_C will come in parallel with the upper resistance R_1 of the biasing network of the next stage. Therefore, the coupling capacitor C_C isolates the d.c. of one stage from the next stage, but allows the passage of a.c. signal.</p>	<p>2 marks – circuit dia.</p> <p>2 marks for expln.</p>
Q3.	Attempt any Four	16
Ans a	<p>Two different mechanism of breakdown are observed in Zener diode. They are 1) Zener breakdown 2) Avalanche breakdown</p> <p>Zener breakdown : Zener breakdown is observed for Zener diodes having breakdown voltage of less than 8 volts. Zener breakdown is observed in heavily doped zener diodes whenever reverse voltage is applied to a heavily doped zener diode, intense electric field is developed across the depletion layer of the zener diode. This heavy electric field breaks covalent bonds and generates large number of electron hole pairs. These large number of charge carriers causes the breakdown of junction of Zener diode. This type of breakdown is referred as zener breakdown and the effect is known as zener effect.</p> <p>Avalanche breakdown : Avalanche breakdown is observed for lightly doped zener diodes having breakdown voltage of greater than 8 volts. Whenever reverse voltage is applied to a lightly doped zener diode, conduction takes place due to movement of minority charge carriers with increased reverse bias, these minority charge carrier acquire more kinetic energy and they collide with the stationary atoms. During this process, they break covalent bonds and generate free electrons. These free electrons also acquire kinetic energy and collide with other atoms to generate more free carriers. Thus in a short time reverse current in a zener diode increases sharply due to presence of large number of free charge carriers. This type breakdown is referred as Avalanche breakdown and the effect is known as avalanche effect.</p>	<p>2</p> <p>2</p>

Ans : d

Transistorized Series Voltage Regulator

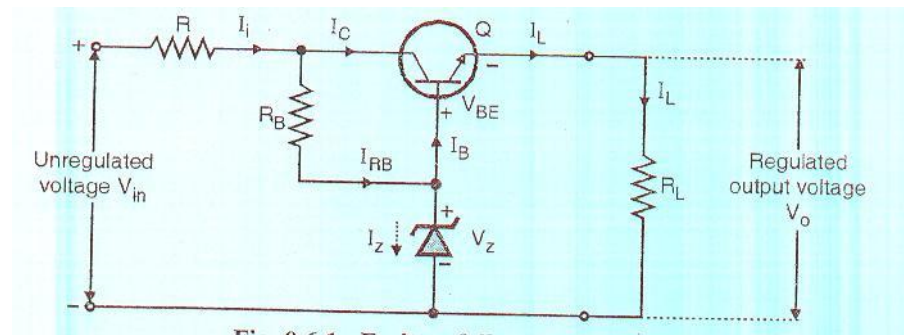Circuit
dia. –
2marks

In this circuit transistor Q acts as a control element. This transistor Q is connected in series with the load hence the circuit is called as Series Voltage Regulator. Other components in the circuit are Zener diode (V_Z), and two resistors R & R_B .

Expln. - 2
marks

Zener diode V_Z is operated in breakdown region and provides constant voltage V_Z .

Resistance R_B provides the limiting current to Zener diode.

The total current in the circuit is decided by resistance R.

As V_Z & V_{BE} of the transistor are constant, output voltage across R_L will also be constant. To find output voltage V_O ,

Applying KVL to o/p loop of the circuit

$$V_{BE} + I_L R_L - V_Z = 0$$

$$\text{Therefore, } V_O = I_L R_L = V_Z - V_{BE}$$

$$V_O = V_Z - V_{BE}$$

As V_{BE} is constant (approx. 0.6V to 0.7V).


Therefore output voltage of this circuit is decided by Zener diode V_Z .




The voltage regulator action can be explained as follows


If $V_O \uparrow \rightarrow V_{BE} \uparrow \rightarrow I_B \uparrow \rightarrow I_C \uparrow \rightarrow I_{RB} \downarrow \rightarrow I_B \downarrow \rightarrow V_{BE} \downarrow \rightarrow V_O \downarrow$ V_O gets regulated


If $V_O \downarrow \rightarrow V_{BE} \downarrow \rightarrow I_B \downarrow \rightarrow I_C \downarrow \rightarrow I_{RB} \uparrow \rightarrow I_B \uparrow \rightarrow V_{BE} \uparrow \rightarrow V_O \uparrow$ & V_O gets regulated.

Ans : e	<p>Amplifier : The circuit which amplifies input signal is called as an amplifier.</p> <p>Classification of amplifier is based on various factors as given below :</p> <ol style="list-style-type: none"> 1. Classification based on purpose of amplification. 2. Classification based on frequency range. 3. Classification based on the position of Q point. 4. Classification depending on the type of coupling. <p><u>1. Classification based on purpose of amplification</u> : Based on the purpose of amplification, the amplifiers are classified as voltage amplifiers or power amplifiers.</p> <p>Voltage amplifiers : The amplifier which is used for amplifying input voltage is called as voltage amplifier.</p> <p>Power amplifier : Power amplifier delivers large power to the load. As $P = I^2 R$, therefore in a power amplifier boosting of current takes place to deliver large power.</p> <p><u>2. Classification based on frequency range</u> : Based on frequency, amplifiers are classified as AF amplifiers and RF amplifiers.</p> <p>AF amplifier : AF amplifier amplifies audio range of frequency signals (20 Hz to 20 KHz)</p> <p>RF amplifier : RF amplifier is an amplifier used for amplifying radio frequency signals (typically more than 100 KHz)</p> <p><u>3. Classification based on the position of Q point</u> : Based on the position of Q point amplifiers are classified as class A, class B, class C and class AB amplifier.</p> <p>Class A amplifier : In class A amplifier the operating point Q is in the centre of active region. This amplifier provides amplification of 360° (both the half cycles).</p> <p>Class B amplifier : In class B amplifier the operating point Q is on the boundary of cut off and active region. This amplifier provides amplification of 180° (one half cycle)</p> <p>Class C amplifier : In class C amplifier the operating point Q is in cut off region. This amplifier provides amplification of less than 180° (less than one half cycle).</p> <p>Class AB amplifier : In class AB amplifier the operating point Q is between centre of active region and starting of active region. This amplifier provides amplification of more than 180° & less than 360°.</p> <p><u>4. Classification depending on the type of coupling</u> : Based on type of coupling, the amplifiers are classified as direct coupled amplifier, RC coupled amplifier and transformer coupled amplifier.</p> <p>Direct Coupled amplifier : The different stages of direct coupled amplifier are directly connected together. Direct coupled amplifier is used for amplifying low frequency signals.</p> <p>RC coupled amplifier: The different stages of RC coupled amplifier are connected together using resistor & capacitor coupling. RC coupled amplifiers are used for amplifying audio frequency signals (20 Hz to 20 KHz)</p> <p>Transformer coupled amplifier : The different stages of transformer couple amplifier are connected together using transformers. Transformer coupled amplifiers are used for amplification of high frequency signals. (Typically more than 100 KHz)</p>	<p>Defn. of amp. 1 mark.</p> <p>Classi of amp – 3 marks</p>
---------	--	---

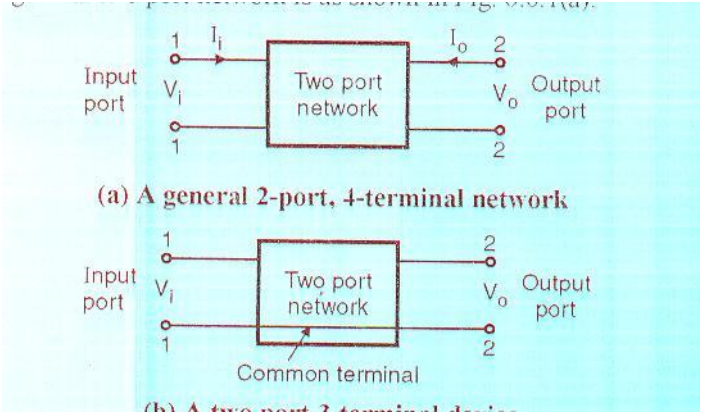Ans : f	<p>Differentiate between BJT & JFET</p> <table border="1"> <thead> <tr> <th>Sr. No.</th><th>BJT</th><th>JFET</th></tr> </thead> <tbody> <tr> <td>1</td><td>Symbol of NPN or PNP transistor</td><td>Symbol of n-channel JFET or P-channel JFET.</td></tr> <tr> <td>2</td><td>BJT is a Bipolar device</td><td>JFET is a unipolar device</td></tr> <tr> <td>3.</td><td>Input impedance is low (In $K\Omega$)</td><td>Input impedance is high (In $M\Omega$)</td></tr> <tr> <td>4</td><td>AC voltage gain of BJT amplifier is high (100-300)</td><td>AC voltage gain of JFET amplifier is low (less than 50)</td></tr> <tr> <td>5</td><td>Transfer characteristics is linear.</td><td>Transfer characteristics of JFET is non linear.</td></tr> <tr> <td>6</td><td>Thermal runaway can damage the BJT.</td><td>Thermal runaway does not take place.</td></tr> <tr> <td>7.</td><td>Noise generated by BJT is high</td><td>Noise generated by JFET is low</td></tr> <tr> <td>8.</td><td>BJT is current controlled device.</td><td>JFET is a voltage controlled device.</td></tr> <tr> <td>9</td><td>BJT is more sensitive</td><td>JFET is less sensitive.</td></tr> <tr> <td>10</td><td>Size of BJT is bigger than JFET</td><td>Size of JFET is smaller than BJT.</td></tr> </tbody> </table>	Sr. No.	BJT	JFET	1	Symbol of NPN or PNP transistor	Symbol of n-channel JFET or P-channel JFET.	2	BJT is a Bipolar device	JFET is a unipolar device	3.	Input impedance is low (In $K\Omega$)	Input impedance is high (In $M\Omega$)	4	AC voltage gain of BJT amplifier is high (100-300)	AC voltage gain of JFET amplifier is low (less than 50)	5	Transfer characteristics is linear.	Transfer characteristics of JFET is non linear.	6	Thermal runaway can damage the BJT.	Thermal runaway does not take place.	7.	Noise generated by BJT is high	Noise generated by JFET is low	8.	BJT is current controlled device.	JFET is a voltage controlled device.	9	BJT is more sensitive	JFET is less sensitive.	10	Size of BJT is bigger than JFET	Size of JFET is smaller than BJT.	Any 4 point – 4 marks.
Sr. No.	BJT	JFET																																	
1	Symbol of NPN or PNP transistor	Symbol of n-channel JFET or P-channel JFET.																																	
2	BJT is a Bipolar device	JFET is a unipolar device																																	
3.	Input impedance is low (In $K\Omega$)	Input impedance is high (In $M\Omega$)																																	
4	AC voltage gain of BJT amplifier is high (100-300)	AC voltage gain of JFET amplifier is low (less than 50)																																	
5	Transfer characteristics is linear.	Transfer characteristics of JFET is non linear.																																	
6	Thermal runaway can damage the BJT.	Thermal runaway does not take place.																																	
7.	Noise generated by BJT is high	Noise generated by JFET is low																																	
8.	BJT is current controlled device.	JFET is a voltage controlled device.																																	
9	BJT is more sensitive	JFET is less sensitive.																																	
10	Size of BJT is bigger than JFET	Size of JFET is smaller than BJT.																																	
Q4.	Attempt any FOUR	16																																	
Ans : a	<p>Two port network</p>  <p>The image contains two circuit diagrams. Diagram (a) shows a 'Two port network' with four terminals. The input port has terminals 1 and 1, with voltage V_i and current I_i entering terminal 1. The output port has terminals 2 and 2, with voltage V_o and current I_o leaving terminal 2. Diagram (b) shows a 'Two port 3-terminal device' where one terminal is common to both the input and output ports. The input port has terminals 1 and 1, with voltage V_i. The output port has terminals 2 and 2, with voltage V_o. The common terminal is labeled 'Common terminal'.</p> <p>(a) A general 2-port, 4-terminal network</p> <p>(b) A two-port 3-terminal device</p> <p>This network has an input port and an output port. Therefore total number of terminals are four.</p> <ul style="list-style-type: none"> - The two port network model is used in mathematical circuit analysis techniques to isolate portions of larger circuits. - For example transistors are often regarded as 2 ports, characterized by their h – parameters. - Transistor consists of 3 terminals. So, one of the three terminals is common to the input and output ports. - Depending on which terminal is made common to input & output port there are three possible configurations of transistors. <ol style="list-style-type: none"> 1) Common Base Configuration 2) Common Emitter Configuration 3) Common Collector Configuration 	<p>Any 1 dia. for 2 marks</p> <p>Expln. – 2 marks</p>																																	

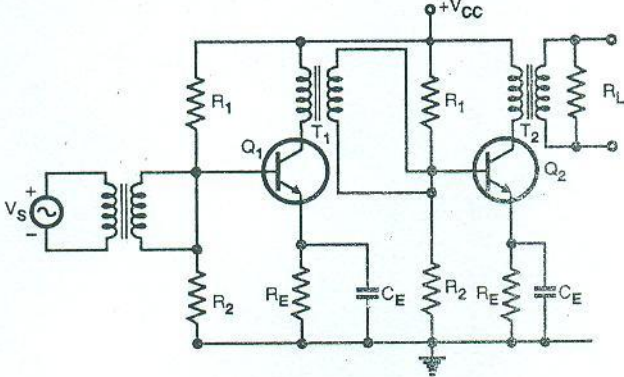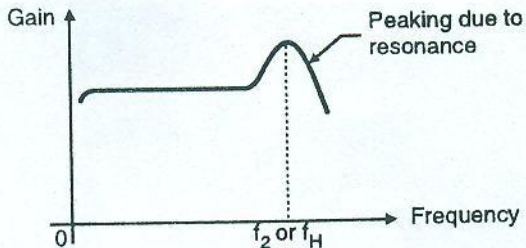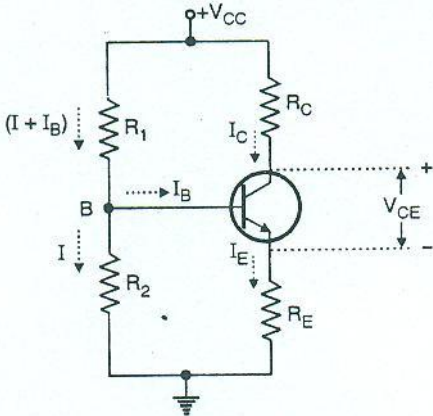Q5	Attempt any FOUR of the following	16
Ans : a	<p>Two stage Transformer Coupled Amplifier.</p>  <p>Frequency Response.</p> 	2
Ans : b	<p>Voltage Divider Bias.</p>  <p>Working : -</p> <p>Figure shows the circuit of a voltage divider bias. It is the most widely used DC biasing circuit. It is commonly known as voltage divider bias or self bias. The name voltage divider is derived from the fact that resistors R_1 and R_2 form a potential divider across the supply V_{CC}. The voltage drop across the resistor R_2 forward biases the base-emitter junction of a transistor. The emitter resistor R_E provides the DC stability. By suitably selecting this voltage divider network, the operating point of the transistor can be made almost independent of current gain β.</p> <p>To set the operating point Q, first determine the base current. To get more accurate value of base current, Thevenin's Theorem is used. Now applying the Thevenin's theorem, we get the voltage,</p>	2

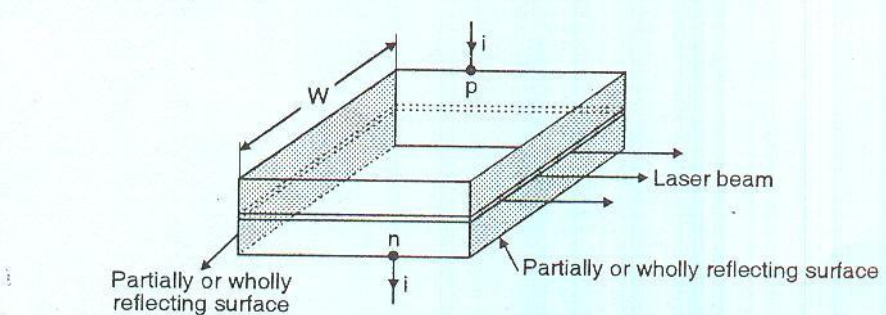
	$V_{TH} = \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{CC}$ <p>And the equivalent resistance.</p> $R_{TH} = R_1 R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$ <p>Applying KVL to the base emitter loop of this circuit,</p> $V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$ $I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E} \quad (I_E = (\beta + 1) I_B)$ $I_B = \frac{V_{TH}}{R_{TH} + \beta R_E} \quad (V_{TH} \gg V_{BE}, (\beta + 1) = \beta)$ $I_C = \beta I_B$ $I_C = \frac{V_{TH}}{R_E + R_{TH} / \beta}$ $I_C = V_{TH} / R_E \quad (R_E \gg R_{TH} / \beta)$ <p>Applying KVL to the output section, we get</p> $V_{CC} = I_C R_C + V_{CE} + I_E R_E$ $V_{CE} = V_{CC} - I_C (R_C + R_E)$	
<p>Ans : c</p>	<p>Laser Diode</p>  <p>Operating Principle :</p> <ul style="list-style-type: none"> ➤ When current is passed through a diode junction light is emitted due to spontaneous emission. ➤ When a critical level is exceeded, the population of minority carries on either sides of the junction increases. This will increase the number of recombinations of electrons and holes and hence the number of Photons emitted. ➤ Thus the density of photons increases to such a level that they start colliding with the already emitted minority carriers. This is called stimulation of the emitted minority carriers. ➤ This gives rise to the so called stimulated emission in which two photons are released instead of one. Both have the same frequency and energy level. ➤ The laser action of the semiconductor diode can be enhanced by placing a reflecting surface on each side of the junction. ➤ It is important to understand that the stimulated emission will take place only when the forward diode current exceeds a minimum level called threshold level. 	<p>2</p> <p>2</p>

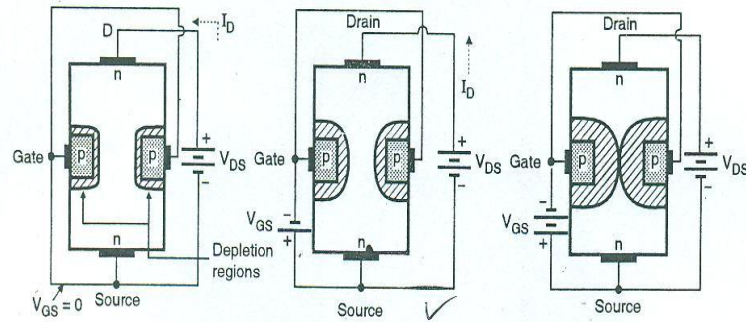




(a) Operation with no bias voltage (b) Operation with a small negative gate source bias (c) Operation with a large negative gate source bias

Operation of n channel JFET :

- i) Operation of n-channel JFET with $V_{GS} = 0$
 - Due to the supply voltage V_{DS} , current starts flowing through the channel.
 - The n-type material has a finite resistance. Therefore the drain current flow, causes a voltage drop along the channel.
 - This voltage drop will reverse bias the gate to source p-n junction.
 - The depletion region of the reverse biased p-n junction penetrates more into the n-type bar because it is lightly doped as compared to the heavily doped p-type gate.
 - The penetration of the depletion region into n-type bar depends on the reverse bias voltage. Due to the depletion regions the width of the channel available for conduction is reduced.
- ii) Operation of a n-channel JFET for small negative V_{GS} :-
 - Due to the reverse voltage applied across the gate source junction, the penetration of the depletion region into n-type material increases further.
 - This will reduce the channel width further. Due to reduced channel width less number of electrons can pass through to drain from source. Therefore, drain current I_D reduces with increase in $-V_{GS}$.
- iii) Operation of n-channel JFET for large value of negative V_{GS} :
 - As the negative voltage V_{GS} is further increased, the depletion region spread more inside the n-type bar.
 - At a certain value of negative V_{GS} , the depletion regions touch each other.
 - The channel width is therefore zero and therefore the drain current $I_D = 0$.
 - Thus with increase in the negative gate to source voltage, the channel becomes more and more narrow and drain current I_D reduces.

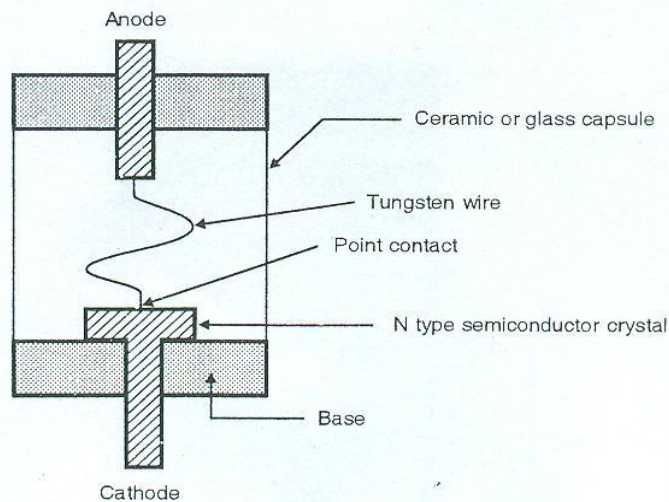Ans : e	First stage voltage gain in dB = $20 \log 100 = 40 \text{ dB}$ Second stage voltage gain in dB = $20 \log 200 = 46.02 \text{ dB}$ Third stage voltage gain in dB = $20 \log 300 = 49.54 \text{ dB}$ The total voltage gain in dB = $40 + 46.02 + 49.54$ = 135.56 dB	4																																													
Ans : f	Comparison between CB, CE and CC <table><tr><th>Sr. No.</th><th>Parameters</th><th>CB</th><th>CE</th><th>CC</th></tr><tr><td>1</td><td>Common terminal between input and output</td><td>Base</td><td>Emitter</td><td>Collector</td></tr><tr><td>2</td><td>Input Current</td><td>I_E</td><td>I_B</td><td>I_B</td></tr><tr><td>3</td><td>Output Current</td><td>I_C</td><td>I_C</td><td>I_E</td></tr><tr><td>4</td><td>Current gain</td><td>$\alpha \text{ dc} = I_C/I_E$</td><td>$\beta \text{ dc} = I_C/I_B$</td><td>$\gamma = I_E/I_B$</td></tr><tr><td>5</td><td>Input Voltage</td><td>V_{EB}</td><td>V_{BE}</td><td>V_{BC}</td></tr><tr><td>6</td><td>Output Voltage</td><td>V_{CB}</td><td>V_{CE}</td><td>V_{EC}</td></tr><tr><td>7</td><td>Voltage gain</td><td>Medium</td><td>Medium</td><td>Less than 1</td></tr><tr><td>8</td><td>Applications</td><td>As preamplifier</td><td>Audio Amplifiers</td><td>For impedance matching.</td></tr></table>	Sr. No.	Parameters	CB	CE	CC	1	Common terminal between input and output	Base	Emitter	Collector	2	Input Current	I_E	I_B	I_B	3	Output Current	I_C	I_C	I_E	4	Current gain	$\alpha \text{ dc} = I_C/I_E$	$\beta \text{ dc} = I_C/I_B$	$\gamma = I_E/I_B$	5	Input Voltage	V_{EB}	V_{BE}	V_{BC}	6	Output Voltage	V_{CB}	V_{CE}	V_{EC}	7	Voltage gain	Medium	Medium	Less than 1	8	Applications	As preamplifier	Audio Amplifiers	For impedance matching.	4 (Any 4 points)
Sr. No.	Parameters	CB	CE	CC																																											
1	Common terminal between input and output	Base	Emitter	Collector																																											
2	Input Current	I_E	I_B	I_B																																											
3	Output Current	I_C	I_C	I_E																																											
4	Current gain	$\alpha \text{ dc} = I_C/I_E$	$\beta \text{ dc} = I_C/I_B$	$\gamma = I_E/I_B$																																											
5	Input Voltage	V_{EB}	V_{BE}	V_{BC}																																											
6	Output Voltage	V_{CB}	V_{CE}	V_{EC}																																											
7	Voltage gain	Medium	Medium	Less than 1																																											
8	Applications	As preamplifier	Audio Amplifiers	For impedance matching.																																											
Q6.	Attempt any FOUR of the following	16																																													
Ans : a	Point Contact Diode  Construction : <ul style="list-style-type: none">➤ The N type semiconductor crystal (Si or Ge) is mounted on the base. A contact is made with this N type crystal and the connection is brought out as cathode.➤ Anode is connected to a stiff pointed tungsten wire, which is placed under pressure in contact with the N type semiconductor crystal.➤ The contact area of this wire with the N type crystal is much smaller than the cross sectional area of the wire.➤ The entire assembly is enclosed in a ceramic or glass capsule.➤ The tungsten wire is coated with indium which acts as an acceptor impurity.➤ The pn junction is formed at the point of contact between the tungsten wire and the n-type semiconductor.	2																																													

Comparison between half wave rectifier and Full wave rectifier		4 (Any 4 points)																																					
Ans : b	<table><tr><th>Sr. No.</th><th>Parameter</th><th>Half wave rectifier</th><th>Full wave rectifier</th></tr><tr><td>1</td><td>TUF</td><td>28.7 %</td><td>69.3 %</td></tr><tr><td>2</td><td>Ripple factor</td><td>121 %</td><td>48 %</td></tr><tr><td>3</td><td>Ripple frequency</td><td>50 Hz</td><td>100 Hz</td></tr><tr><td>4</td><td>Number of diodes used</td><td>One</td><td>Two or Four</td></tr><tr><td>5</td><td>PIV</td><td>Vm</td><td>2 Vm</td></tr><tr><td>6</td><td>RMS load voltage V_{Lrms}</td><td>Vm / 2</td><td>Vm / √ 2</td></tr><tr><td>7</td><td>RMS load current I_{Lrms}</td><td>Im / 2</td><td>Im / √ 2</td></tr><tr><td>8</td><td>DC load current I_{L dc}</td><td>Im / π</td><td>2 Im / π</td></tr></table>	Sr. No.	Parameter	Half wave rectifier	Full wave rectifier	1	TUF	28.7 %	69.3 %	2	Ripple factor	121 %	48 %	3	Ripple frequency	50 Hz	100 Hz	4	Number of diodes used	One	Two or Four	5	PIV	Vm	2 Vm	6	RMS load voltage V _{Lrms}	Vm / 2	Vm / √ 2	7	RMS load current I _{Lrms}	Im / 2	Im / √ 2	8	DC load current I _{L dc}	Im / π	2 Im / π		
Sr. No.	Parameter	Half wave rectifier	Full wave rectifier																																				
1	TUF	28.7 %	69.3 %																																				
2	Ripple factor	121 %	48 %																																				
3	Ripple frequency	50 Hz	100 Hz																																				
4	Number of diodes used	One	Two or Four																																				
5	PIV	Vm	2 Vm																																				
6	RMS load voltage V _{Lrms}	Vm / 2	Vm / √ 2																																				
7	RMS load current I _{Lrms}	Im / 2	Im / √ 2																																				
8	DC load current I _{L dc}	Im / π	2 Im / π																																				
Ans : c	DC Load line	2																																					
<p>DC load line</p> <ul style="list-style-type: none">➤ The DC word indicates that this line is drawn under the dc operating conditions without any ac signal at the input.➤ And the word load line is used because the slope of this line is – 1/RC where RC is the load resistance. <p>Operating Point</p> <ul style="list-style-type: none">➤ It is the point on the load line which represents the dc current through a transistor (ICQ) and the voltage across it (VCEQ) when no ac signal is applied.➤ The dc load line is a set of infinite number of such operating points and the user or designer can choose any point on the dc load as the operating point.➤ The position of operating point on the load line is dependent on the application of the transistor.➤ The factors affecting the stability of Q-point are : 1. Changes in temperature 2. Changes in the value of β_{dc} .																																							
		2																																					

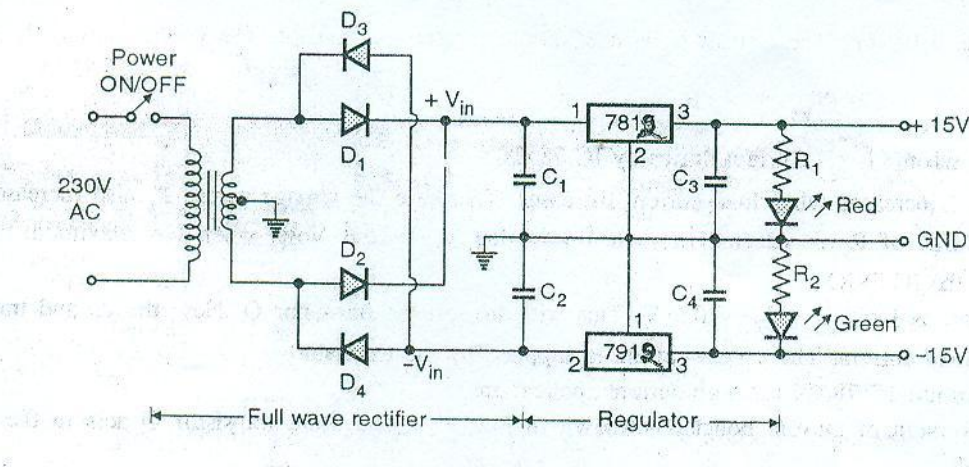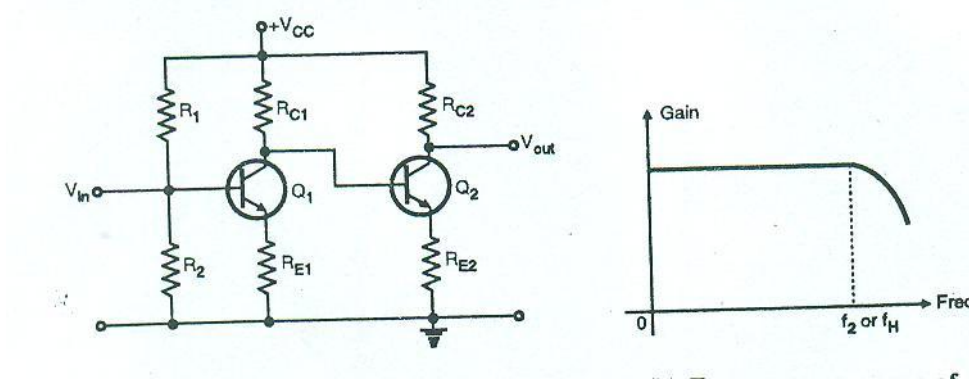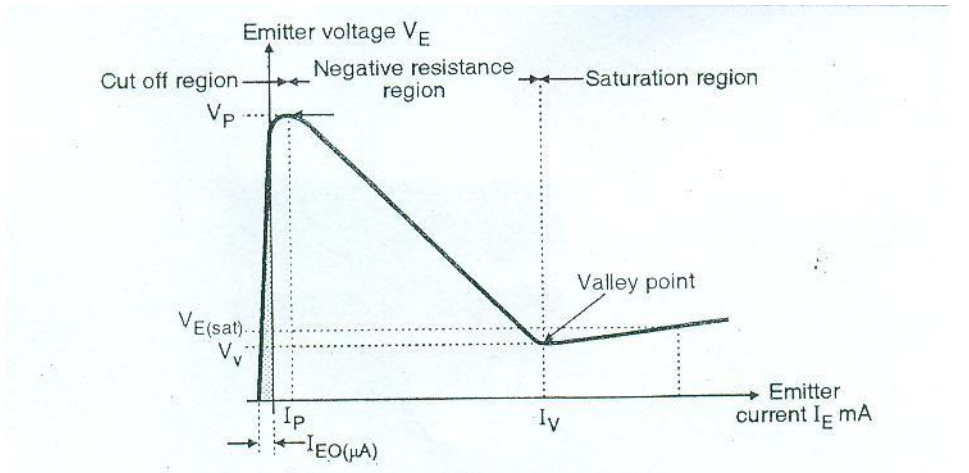Ans : d	<p>Dual Power Supply</p> 	4
Ans : e	<p>Two stage Direct Coupled Amplifier</p>  <p>Advantages : (any 2)</p> <ol style="list-style-type: none"> 1) Wide frequency response (large Bandwidth) 2) Reduced cost and complexity due to absence of coupling capacitors. 3) This amplifier can amplify even the dc signals. <p>Disadvantages : (any 2)</p> <ol style="list-style-type: none"> 1) The output waveform has a dc shift. 2) Poor frequency response at higher frequencies. 3) Poor temperature stability. 	2
Ans : f	<p>UJT Characteristics</p>  <p>(Contd pg. 21)</p>	2

	<p>V_P (Peak Point Voltage) The emitter voltage, at which the emitter current suddenly increases, is called the Peak Point Voltage.</p> <p>OR The emitter voltage at which the UJT turns ON is called as the Peak Voltage.</p> <p>V_V (Valley Point Voltage) The emitter voltage, at which the emitter current is driven into saturation is called Valley Point Voltage.</p>	1
		1